



(Pages : 2)

8071

Reg. No. :

Name :

Fourth Semester B.Tech. Degree Examination, December 2009
(2003 Scheme)
03.402: SOLID STATE DEVICES AND CIRCUITS (E)

Time : 3 Hours

Max. Marks : 100

Instruction: Answer all questions from Part A and any three questions from Part B choosing not more than one question from each module.

PART – A

1. Prove that the collector current of the transistor in the active region in CE configuration is $I_C = \beta I_B + (1 + \beta) I_{CO}$.
2. What are the factors concerned for drifting of the operating point of a transistor amplifier ?
3. For a N- channel JFET $I_{DSS} = 16\text{mA}$, $V_P = 6\text{V}$, $G_{mo} = 4000 \text{ ps}$. Calculate the drain current and trans conductance at $V_{GS} = -4\text{V}$.
4. Explain the working of a class C amplifier and give an application.
5. Determine the voltage gain, input and output impedance for voltage series feed back having $A = -100$, $R_i = 100 \text{ k}\Omega$, $R_o = 20\text{k}\Omega$ for feed back with $B = -0.1$.
6. Explain why crystal oscillator have very high frequency stability.
7. What is meant by drift compensation ?
8. Define slew rate of an opamp.
9. Explain how opamp is used as integrator.
10. What is the effect of noise on zero crossing detector. (4×10=40 Marks)

P.T.O.

**Module – I**

11. a) What is the need of bias compensation in transistor amplifiers and with a neat sketch explain one method of Bias compensation.
- b) Draw the equivalent circuit of a transistor amplifier in CB configuration using h parameters and derive expressions for current gain, input impedance, voltage gain, output admittance and power gain.
12. a) Draw a self biased JFET common source amplifier and explain its operation.
- b) Derive an expression for the voltage gain of a source follower JFET amplifier with a drain resistance R_p .

Module –II

13. a) Draw the circuit diagram of a transformer coupled amplifier and explain the function of each of the components used. Plot its frequency response.
- b) Explain the operation of a series fed class A amplifier and obtain the expression for over all efficiency. Also find the maximum efficiency.
14. a) Discuss about the factors responsible for causing distortion in amplifiers.
- b) What is negative feed back and how it will improve the stability of an amplifier ? Explain the working of an RC phase shift oscillator.

Module – III

15. a) Compare the characteristics of 741 and 301 IC operational amplifiers.
- b) An amplifier with $2.2 \text{ K}\Omega$ input resistance and $40 \text{ k}\Omega$ output resistance has a voltage gain of 80. The amplifier is modified to provide 15% negative feed back in series with the input. Calculate
- i) Voltage gain with feed back
- ii) R_{if} and R_{of}
16. a) Discuss the necessity for frequency compensation in opamps.
- b) Explain how an op-amp can be used as a voltage level detector. List the important characteristics of a comparator. **(3×20=60 Marks)**
-