

**MCA (Revised)**  
**Term-End Examination**  
**June, 2007**

**MCS-012 : COMPUTER ORGANISATION &  
ASSEMBLY LANGUAGE PROGRAMMING**

Time : 3 hours

Maximum Marks : 100

(Weightage 75%)

---

**Note :** Question no. 1 is **compulsory** and carries 40 marks. Attempt any **three** questions from the rest.

---

---

1. (a) Simplify the following boolean function using Karnaugh map method :  
$$F(A, B, C, D) = \Sigma(1, 2, 5, 6, 7, 8, 9, 11, 12, 15)$$
  
Also, draw the corresponding logic circuit diagram. 8
- (b) Design and draw a  $3 \times 8$  decoder using NOT gates and AND gates and explain its working. 8
- (c) Design a circuit to interface four RAMs of  $128 \times 8$  size and a ROM of  $512 \times 8$  size. Draw the memory map for the same. 8

- (d) Write an assembly language procedure for 8086 microprocessor that divides a 32-bit number by a 16-bit number. The procedure should be written in general, so that it may be defined in one module and can be called in any other module. 10
- (e) List all the features of the RISC architecture. 6
2. (a) Write an assembly language program for 8086 microprocessor to sort a given list of 5 numbers in ascending order and explain its logic. 10
- (b) Design and draw a master-slave flip flop using JK flip flops. What are the advantages it offers over other flip flops ? 10
3. (a) Find the following : 9
- (i) 9's complement of  $0342_{(10)}$
- (ii) 10's complement of  $0342_{(10)}$
- (iii) 2's complement of  $1100110_{(2)}$
- (b) Explain the basic principle of Quine-McCluskey method of simplifying the boolean expression with the help of an example function. 6
- (c) Design and draw the 4-bit adder-subtractor circuit using full adders and XOR gates. Explain its working in brief. 5

4. (a) Give the Excitation tables and Block diagrams for the following : 10
- (i) D flip-flop
  - (ii) T flip-flop
- (b) Write an assembly program to concatenate two strings of size 3 characters and explain its logic. 10
5. Explain the following : 5×4=20
- (i) Flash memory
  - (ii) Direct Memory Access (DMA)
  - (iii) Jaz drive
  - (iv) Instruction pipelining
  - (v) Hardwired control organization

