

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**BE - SEMESTER-III (New) EXAMINATION – WINTER 2015**

**Subject Code:2130902****Date:21/12/2015****Subject Name: Analog Electronics****Time: 2:30pm to 5:00pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
- 4.

MARKS

- |            |   | MARKS     |
|------------|---|-----------|
| <b>Q.1</b> | <b>Short Questions</b>  | <b>14</b> |
| 1          | What is the function of silicon dioxide layer in MOSFETS?   |           |
| 2          | A JFET is _____ (a) current controlled device (b) Voltage controlled device (c) has high gate current (d) none of above   |           |
| 3          | An enhancement mode MOSFET is off when the gate voltage is _____ (a) zero (b) less than threshold value (c) negative (d) none of above  |           |
| 4          | Calculate the output voltage of a non inverting amplifier for values of $V_1 = 2V$ , $R_f = 500 K\Omega$ , $R_1 = 100 K\Omega$  |           |
| 5          | Integrator is basically _____ filter. (a) Low Pass (b) High Pass (c) Band Pass (d) Band Reject  |           |
| 6          | Which multivibrator is basically a flip flop?   |           |
| 7          | IC 555 needs to be operated in _____ mode for timer operation.  |           |
| 8          | For input of a square wave to a differentiator, its output will be _____ (a) sine wave (b) triangular wave (c) spikes   |           |
| 9          | Write the main advantage of precision rectifier compared to diode rectifier.  |           |
| 10         | Why is the speed of response of schmitt trigger is higher than conventional comparator?   |           |
| 11         | The phase shift between input and output of a voltage follower is _____   |           |
| 12         | IC 741 has a Unity Gain Bandwidth at gain _____ and frequency _____   |           |
| 13         | _____ is the fixed negative voltage regulator in series. (a) 79XX (b) 78XX (c) LM337 (d) LM 317.  |           |
| 14         | What are the Barkhausen condition for oscillations to occur?  |           |
| <b>Q.2</b> | (a) Explain the following terms. (1) PSRR (2) Input bias current (3) Input offset Voltage   | <b>03</b> |
|            | (b) Determine the output voltage of an op-amp for input voltages of $V_{i1} = 150 \mu V$ , $V_{i2} = 140 \mu V$ . The amplifier has a differential gain of $A_d = 4000$ and the value of CMRR is: (a) 100. (b) $10^5$ . | <b>04</b> |
|            | (c) Mention the biasing circuit used for the depletion MOSFET.  | <b>07</b> |
|            | <b>OR</b>   |           |
|            | (c) What will be effect of voltage series feedback amplifier on input resistance, gain and stability?   | <b>07</b> |
| <b>Q.3</b> | (a) Explain how an OP-AMP works as an averaging amplifier?  | <b>03</b> |
|            | (b) Explain the effect of negative feedback on frequency response in an   | <b>04</b> |

- OP-AMP.
- (c) What do you mean by slew rate in an OP-AMP? Also mention about causes of slew rate and explain its significance in applications. **07**
- OR**
- Q.3** (a) Draw and explain OP-AMP as a zero crossing detector. Give suitable example of its practical application. **03**
- (b) What are the requirements of Instrumentation amplifier for practical purpose? **04**
- (c) Explain the working of a practical integrator circuit with neat sketch. Also draw output waveforms for sinusoidal and square wave inputs. **07**
- Q.4** (a) Describe how an Op-amp may be used as voltage to current converter. **03**
- (b) State the application of OP-AMP based Wein bridge oscillator. **04**
- (c) Explain circuit diagram of OP- AMP as a Peak detector. **07**
- OR**
- Q.4** (a) Draw the IC-555 based monostable multivibrator circuit. **03**
- (b) What are the applications of OP- AMP based schmitt trigger circuit. **04**
- (c) Explain with circuit diagram the operation of a VCO. **07**
- Q.5** (a) Compare between active and passive filters. **03**
- (b) Explain with the help of circuit diagram, the operation of second order Butterworth high pass filter. **04**
- (c) Design first order low pass filter for the following specifications. **07**  
 (1) Passband voltage gain=2 (2) Cut-off frequency  $f_c=10$  KHz..
- OR**
- Q.5** (a) Draw and explain typical connection diagram of LM 317 IC. **03**
- (b) Explain any one application of PLL **04**
- (c) Design IC 555 based astable multivibrator having an output frequency of 5 KHZ with 70% duty cycle. **07**

\*\*\*\*\*