

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**BE - SEMESTER-III (New) EXAMINATION – WINTER 2015**

**Subject Code:2131004****Date:18/12/2015****Subject Name: Digital Electronics****Time: 2:30pm to 5:00pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1 Short Questions 14**
- 1 Convert decimal number  $(43)_{10}$  to binary.
  - 2 Convert octal number  $(234)_8$  to hexadecimal.
  - 3 Which gates are also known as controlled NOT gate?
  - 4 Bubbled OR is also called \_\_\_\_\_.
  - 5 How many selection lines are required in  $32 \times 1$  MUX?
  - 6 How many enable lines are there in  $3 \times 8$  decoder IC 74138?
  - 7 Define fan-out.
  - 8 Which flip-flop is also known as *ones-catching* flip-flop?
  - 9 Which circuit is used to eliminate *chattering*?
  - 10 Which latch is also known as *transparent* latch?
  - 11 Calculate the number of state flip-flops required to generate 49 states?
  - 12 Mention two different methods used to delay the state changes sufficiently.
  - 13 What do you mean by conditional output?
  - 14 What are the advantages of asynchronous state machines?
- Q.2 (a) Convert decimal number  $(0.252)_{10}$  to binary with an error less than 1 %. 03**
- (b) Minimize the following Boolean expressions. 04**
1.  $X = ((A'B'C)' + (A'B)')$
  2.  $Y = AB + ABC' + A'BC + A'BC'$
- (c) Implement following logic function using  $8 \times 1$  MUX. 07**
- $$F = \sum m(0, 1, 3, 5, 7, 11, 13, 14, 15)$$
- OR**
- (c) Design a full adder using  $3 \times 8$  decoder followed by gates. 07**
- Q.3 (a) Draw & explain in brief pin diagram of 7485 four-bit magnitude comparator. 03**
- (b) Using D as the MEV, reduce  $Y = A'B'C'D' + A'B'CD' + AB'C'D' + AB'CD + AB'CD' + AB'CD'$ . 04**
- (c) Minimize following Boolean function using K-map & design the simplified function 07**
- using logic gates.
- $$F = \sum m(1, 2, 4, 6, 7, 11, 15) + \sum d(0, 3)$$
- OR**
- Q.3 (a) Draw a frequency divider using JK FFs to divide input clock frequency by a factor of 8. 03**
- (b) Reduce following Boolean function and then realize the reduced one using NOR gate 04**
- only.
- $$X = A(B'+C)(A+D)$$

- (c) For the figures 1, 2, & 3, plot the output waveforms referenced to the clock signal **07**  
 assuming the initial contents of all FFs is  $Q = 0$ . Assume all FFs are edge triggered.

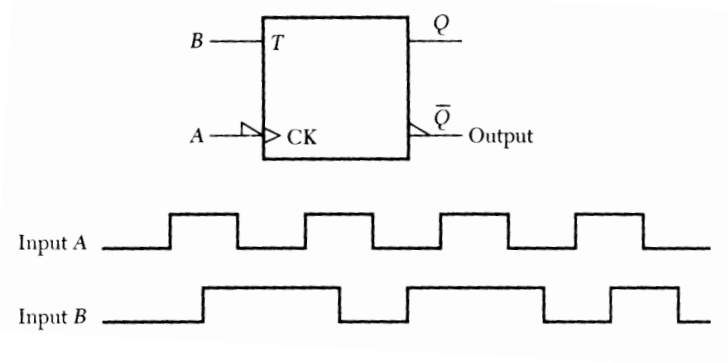


Fig. 1

 


Fig. 2

 


Fig. 3

- Q.4 (a)** Draw a general model for a sequential or state machine. Also list out various types of FSMs. **03**

- (b)** 1. Fill in values for S & R to cause the Q values of the SR FF given in figure 4. **04**

	$t_0$	$t_1$	$t_2$	$t_3$
S	0			
R	0			
Q	1	0	0	1

Fig. 4

2. Plot the output waveform for the inputs shown in figure 5, assuming the initial contents of the FF is  $Q = 0$ .

 


Fig. 5

- (c) Design a 3-bit synchronous up counter using K-maps and positive edge-triggered JK FFs. **07**

**OR**

- Q.4** (a) Draw & explain in brief a high assertion input SR latch. **03**  
 (b) Construct next state table for the state diagram given in figure 6. **04**

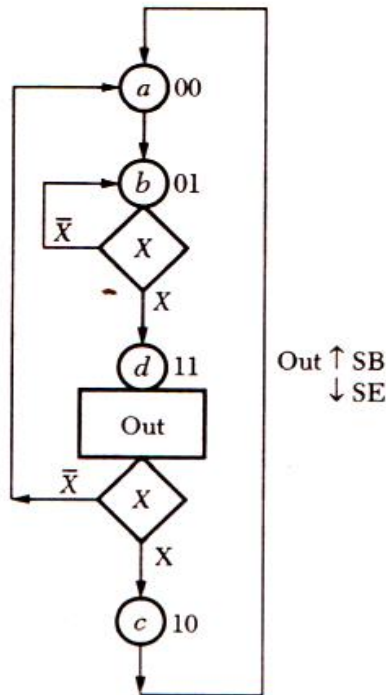


Fig. 6

- (c) What do you mean by an output glitch problem? Explain any one method to eliminate the glitch from an OFL circuit. Draw suitable waveforms and logic diagrams. **07**

- Q.5** (a) Draw & explain in brief general architecture of Xilinx FPGA. **03**  
 (b) Explain *critical race* problem of an asynchronous state machines with the help of one example. **04**  
 (c) Implement following functions using ROM. **07**

$$F1 = \sum m(1, 3, 4, 6)$$

$$F2 = \sum m(2, 4, 5, 7)$$

$$F3 = \sum m(0, 1, 5, 7)$$

$$F4 = \sum m(1, 2, 3, 4)$$

**OR**

- Q.5** (a) With the help of next state D input maps given in figure 7, construct IFL using MUXs of suitable size and number. **03**

 


Fig. 7

- (b) Explain *oscillation* problem of an asynchronous state machines with the help of one example. **04**
- (c) Compare TTL, ECL, & CMOS logic families. **07**

\*\*\*\*\*