

GUJARAT TECHNOLOGICAL UNIVERSITY
BE - SEMESTER-III (New) EXAMINATION – WINTER 2015

Subject Code:2132003**Date:18/12/2015****Subject Name: Design Concepts In Basic Electronics****Time: 2:30pm to 5:00pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1 (a) 14**
- 1 Convert $(3254.64)_8$ into equivalent Binary and Hexadecimal.
 - 2 Following arithmetic operation is correct for the base x. Find base x.


$$(21)_x + (44)_x + (32)_x + (13)_x = (143)_x$$
 - 3 Represent $(786)_{10}$ and $(75)_{10}$ in equivalent BCD and add them showing BCD arithmetic.
 - 4 If we want to implement 2 function at the same time what must be used out of decoder and multiplexer for the implementation.
 - 5 Why look ahead carry generator is required?
 - 6 Explain the importance of Gray code.
 - 7 State points of difference between BCD and binary code.
 - 8 Define peak inverse voltage of diode
 - 9 What do you mean by ideal diode?
 - 10 Why a filter circuit is required after rectifier?
 - 11 What are the parameter on which current gain of transistor depends?
 - 12 With help of output curve of transistor explain load line and Q point.
 - 13 If transistor is to be operated as switch where must be the Q point located.
 - 14 What is voltage multipliers?
- Q.2 (a) 03** With circuit diagram and output waveform explain working of full wave bridge rectifier
- (b) 04** Give the points of difference between half wave, Full wave, and Bridge rectifier.
- (c) 07** Simplify the following Boolean function using Karnaugh map method and realize with minimum NOR gates only.
 $F(A,B,C,D) = \sum (0,1,3,7,13,15) + d(2,11,12,14)$
- OR**
- (c) 07** Design a combinational logic to convert given BCD to seven segment display LED.
- Q.3 (a) 03** Draw and explain internal construction of encoder.
- (b) 04** Implement the following function with help of 8x1 Multiplexer.
 $F(A,B,C,D) = \sum (0,1,3,4,8,9,15)$
- (c) 07** Compare in detail RTL, DTL, TTL, ECL and CMOS.
- OR**
- Q.3 (a) 03** Write the points of difference between combinational and sequential logic.

- (b) Draw the circuit diagram of D-type positive edge triggered flip flop **04**
 (c) Write a note on collector to base bias. **07**
- Q.4** (a) What is ripple counter? **03**
 (b) Explain in detail bidirectional shift register with parallel load **04**
 (c) Discuss with example approximate analysis of the voltage divider bias. **07**

OR

- Q.4** (a) Why we require master slave or edge triggered flip flop **03**
 (b) Design 3-bit up synchronous counter. **04**
 (b) Write the points of comparison between CB, CE and CC configuration of transistor. **07**

 - Q.5** (a) What is energy band diagram? **03**
 (b) Explain the different types of clipping circuits **04**
 (c) The fixed bias circuit of Fig. uses a silicon transistor. The component values are $R_C = 500 \Omega$ and $R_B = 100 \text{ k}\Omega$. β_{dc} of the transistor is 100 at 30°C and increases to 120 at a temperature of 80°C . Determine the percent change in the Q point values over this temperature range. Assume that V_{BE} and I_{CBO} remain constant. **07**



OR

- Q.5** (a) Explain the requirement of compliment in digital logic. **03**
 (b) Explain with circuit diagram positive clamper and negative clamper. **04**
 (c) Explain DC load line and Q-point for any transistor configuration. Also state the necessity of biasing and list biasing methods for transistor **07**
