



17524

15116

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :** (1) *All questions are compulsory.*
(2) *Answer each section on same/separate answer sheet.*
(3) *Answer each next main question on a new page.*
(4) *Illustrate your answers with neat sketches wherever necessary.*
(5) *Figures to the right indicate full marks.*
(6) *Assume suitable data, if necessary.*
(7) *Use of Non-programmable Electronic Pocket Calculator is permissible.*

Marks

1. A) Attempt **any three** :

(4×3=12)

- Define : 1) amplitude 2) cycle 3) form factor 4) peak factor.
- With the help of neat diagram explain concept of single turn alternator.
- Explain insulated and ground return system.
- State difference between intrinsic and extrinsic semiconductor.

B) Attempt **any one** :

(6×1=6)

- Two resistance of $12\ \Omega$ and $28\ \Omega$ are connected in series and the combination is connected in series with a $10\ \Omega$ resistance. If this combination of resistors is put across 40v d.c. supply, find the current in $12\ \Omega$ and $28\ \Omega$ resistors.
- With the help of neat diagram explain the wiring of headlight and turn indicator and their function.

2. Attempt **any four** :

(4×4=16)

- With the help of neat diagram. Explain self inductance and mutual inductance.
- Define and draw symbols of EMF, Current, Resistance and Capacitance.
- Draw labelled diagram and DC shunt motor. State its two application.
- Explain working of SCR and draw its characteristics. (V – I)
- What is difference between LVDT and RVPT, give any four point.
- With the help of diagram, explain working of FWR also draw relevant waveform.

P.T.O.

**Marks**

- 3. Attempt any four :** **(4×4=16)**
- a) Define : a) Sensitivity b) Resolution c) linearity d) repeatability. 4
 - b) Draw symbol of photodiode and LED also state two application each. 4
 - c) Draw symbol of NOR and NAND gate also draw truth table for each. 4
 - d) State Fleming's righthand rule and lefthand rule. 4
 - e) With neat diagram explain contactless type inductive tachometer. 4
- 4. A) Attempt any three :** **(4×3=12)**
- a) Compare core type and shell type transformer.
 - b) What are the advantages of positive return wiring system ?
 - c) Explain working of ultrasonic flow meter.
 - d) The no. of turns of CV winding of 150 KVA, 50Hz and 115V/230V IQ transformer is 36, calculate : 1) Peak value of Q_m 2) IFL on LV side 3) No. of turns on HV side.
- B) Attempt any one :** **(6×1=6)**
- a) Draw symbol of PNP and NPN transistor. What is difference between PNP and NPN any two ? How transistor worked as amplifier ?
 - b) What is meant by demultiplexer ? Explain its working with neat block diagram also draw schematic diagram.
- 5. Attempt any four :** **(4×4=16)**
- a) Explain working principle of piezo-electric transducer.
 - b) Why single phase motor is not self starting ? How can it be started ?
 - c) Compare zener diode and P-N junction diode with following point :
 - 1) construction
 - 2) symbol
 - 3) characteristics
 - 4) application.
 - d) Give constructional difference between thermistor and RTD any two point.
 - e) What is principle of stroposcope ? Draw symbol of D flip-flop and give its truth table.
- 6. Attempt any four :** **(4×4=16)**
- a) Explain working principle of stepper motor.
 - b) With neat diagram explaining working of shift register.
 - c) What is the necessity of filter and give different types of filter ?
 - d) A sinusoidal waveform is represented by $V = 41.44 \sin (2\pi \omega t + \frac{\pi}{2})$
Find out : 1) amplitude 2) frequency 3) time period 4) angular velocity.
 - e) Draw a neat labelled diagram of RTD and state its operating principles.
-