



17541

15116

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All questions are **compulsory**.
 - (2) Answer **each** next main question on a **new** page.
 - (3) Illustrate your answers with **neat** sketches **wherever** necessary.
 - (4) Figures to the **right** indicate **full** marks.
 - (5) Assume suitable data, if **necessary**.

Marks

1. a) Answer **any three** :

(3×4=12)

- 1) Describe turn ON and turn OFF method for MCT.
- 2) Describe the effect of duty cycle on chopper output voltage.
- 3) Draw the circuit diagram of Half bridge inverter with resistive load. Draw its voltage and current waveform.
- 4) Compare servo type and solid state type stabilizer w.r.t operating principle, efficiency, distortion and applications.

b) Answer **any one** :

(1×6=6)

- 1) Describe the working of Class A chopper using SCR with circuit diagram and waveforms.
- 2) Draw the circuit diagram of push pull inverter with RL load. Describe its working.

2. Answer **any two** :

(2×8=16)

- 1) Draw 3-SCRs series connections diagram. Describe the roll of static and dynamic equalizing n/w. State the need of series and parallel connection of SCR.
- 2) Compare ON-line and OFF line UPS w.r.t. Input voltage, DC voltage, output freqn. applications, distortion, output w/f transient recovery.
- 3) Draw block diagram of sequential timer for resistance welding. Describe the function of each block. List different signals generated.

3. Answer **any four** :

(4×4=16)

- 1) Describe how SCR can be protected from over current with suitable labelled diagram.
- 2) Draw the circuit diagram and explain the working of isolated SMPS.
- 3) Draw the block diagram of line interactive UPS. Describe its working.
- 4) Draw and describe the working of Class-C chopper using SCRs with proper w/fs.
- 5) Draw the block diagram of AC resistance welding and describe it.

P.T.O.



4. a) Answer **any three** :

(3×4=12)

- 1) Describe the operation of Morgan's chopper with ckt diagram.
- 2) Draw and describe the working of relay type stabilizer with diagram.
- 3) Describe the need of protection circuits for power devices. List different types of protection circuits.
- 4) State different PWM techniques used in inverter. Describe any two.

b) Answer **any one** :

(1×6=6)

- 1) Describe how output voltage and harmonics can be controlled using PWM control method of inverter ?
- 2) Draw the circuit diagram of parallel connections of two thyristors and describe with forward characteristics.

5. Answer **any two** :

(2×8=16)

- 1) State the need of energy storage resistance welding. Describe the working of capacitor energy storage welding with wave forms.
- 2) Draw the circuit diagram of phase control method used in AC voltage stabilizer. Describe its operations. List any two adv. and disadv. and any two applications of it.
- 3) Draw and describe the working of Jones chopper with proper waveforms.

6. Answer **any four** :

(4×4=16)

- 1) Draw the constructional diagram of SIT and describe its operation.
 - 2) Draw the Off line UPS and describe the function of each block.
 - 3) With neat diagram describe the principle of resistance welding.
 - 4) Compare half bridge and push pull inverter w.r.t. Use of power device, use of O/P transformer, load voltage and load current.
 - 5) Draw Mc-Murray Bedford inverter with resistive load and describe the working.
-