

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**BE – SEMESTER – VI (OLD).EXAMINATION – WINTER 2016**

**Subject Code: 160905****Date: 24/10/2016****Subject Name: Electrical & Electronic Measurement****Time: 10:30 AM to 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q-1 (a) Explain Maxwell's bridge for measurement of self inductance. 07  
 (b) Explain following term 07  
 1 Accuracy 2. Precision. 3. Sensitivity 4. Resolution
- Q-2 (a) The four arms of bridge are as per given 07  
 Arm AB : capacitor  $C_1$  with internal resistor  $r_1$   
 Arm BC: Non inductive resistance of  $R_3=2000\text{Ohm}$ .  
 Arm CD: Non inductive resistance of  $R_4=2850\text{Ohm}$   
 Arm DA: capacitor  $C_2= 0.5\text{micro F}$ , internal resistance  $r_2=0.4\text{Ohm}$  and  
 Resistor  $R_2=4.8\text{Ohm}$ .  
 Supply frequency 450Hz between A and C and detector between B and D.  
 For balance by above component. Find out capacitance  $C_1$  and internal  
 resistor  $r_1$  and also the dissipating factor for the capacitor.  
 (b) Explain Anderson's Bridge. 07
- OR
- (b) An Owen's bridge is used to measure the properties of a sample sheet  
 steel at 2 kHz . At balance, arm ab is test specimen; arm bc is  $R_3 =100\Omega$ ;  
 arm cd is  $C_4 =0.1\mu\text{F}$  and arm da is  $R_2= 834$  in series with  $C=0.124 \mu\text{F}$  .  
 Determine balance condition and calculate the effective impedance of the  
 specimen under test condition. 07
- Q-3 (a) What are the different difficulties encountered in the measurement of high 07  
 resistance? Explain how these difficulties are over come.  
 (b) Draw the circuit of a Wheatstone bridge and derive the condition of 07  
 balance.
- OR
- (a) Explain megger for high resistance measurement 07  
 (b) Draw the circuit of Kelvin's double bridge used for measurement of low 07  
 resistance. Derive the condition for balance
- Q-4 (a) Explain Flux meter with suitable diagram. 07  
 (b) Explain Murray loop test for location cable fault. 07
- OR
- (a) Describe the method for determination of B-H curve of magnetic material. 07  
 (b) Discuss principle and working of digital LCR meter. 07
- Q-5 (a) Explain construction and working of current transformer. 07  
 (b) Explain harmonic distortion analyzer. 07
- OR
- (a) Derive equation for ratio and phase angle error of a potential transformer 07  
 (b) Explain Hetrodyne wave analyzer. 07

\*\*\*\*\*