



# 17321

16117

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :** (1) *All questions are compulsory.*  
(2) *Answer each next main question on a new page.*  
(3) *Illustrate your answers with neat sketches wherever necessary.*  
(4) *Use of Non-programmable Electronic Pocket Calculator is permissible.*  
(5) *Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.*

**Marks**

1. A) Attempt **any six** of following :

**12**

- Draw symbol of P-N diode, Zener diode.
- Define the term rectification efficiency and rectifier.
- List the types of Biasing in BJT.
- Draw output characteristics showing different region in CE configuration.
- Define the term voltage regulation factor state need of voltage regulation.
- Draw pin configuration of IC 723.
- Draw symbol of NAND Gate and NOR Gate.
- Convert :
  - $(456)_D = ( )_B$
  - $(5A)_H = ( )_D$

B) Attempt **any two** of following :

**8**

- Compare intrinsic and extrinsic semiconductor (any 4 points).
- Explain full wave bridged rectifier with the help of circuit diagram and input output waveform.
- Explain working of n-p-n transistor in unbiased condition.

2. Attempt **any four** of following :

**16**

- List specification of zener diode (any 4).
- Compare half wave rectifier, full wave centre tapped rectifier and full wave bridge rectifier w.r.t.
  - Efficiency
  - Ripple factor
  - TUF
  - Output waveform
- Explain R-C coupled amplifier with circuit diagram.
- Explain construction of n-channel JFET with neat sketch.

**P.T.O.**



- e) Compare CE, CB, CC w.r.t. to
- |                    |                     |
|--------------------|---------------------|
| 1) Current gain    | 2) Voltage gain     |
| 3) Input impedance | 4) Output impedance |
- f) Explain with circuit diagram operation of zener diode as voltage regulator.

**3. Attempt any four of following :** **16**

- Draw experimental circuit diagram and characteristics for forward biased P-N junction diode.
- Explain with circuit diagram fixed bias method of BJT.
- Draw and explain VI characteristics of UJT.
- Draw and explain working principle of N-channel enhancement MOSFET.
- Draw block diagram of DC regulated power supply state function of each block.
- Explain NAND gate as universal gate implement AND, OR and NOT gate using NAND gate only.

**4. Attempt any four of following :** **16**

- Explain operating principle of LASER.
- Explain class B push pull power amplifier with circuit diagram.
- Draw input and output characteristics of CB configuration.
- Explain with circuit diagram transformer coupled amplifier.
- Draw and explain output characteristics of JFET.
- Explain with circuit diagram transistorised series voltage regulator.

**5. Attempt any four of following :** **16**

- Compare BJT with FET (any 4 pts.).
- State the need of multistage amplifier. Draw frequency response of R-C coupled amplifier.
- Draw circuit diagram of voltage divider biasing list two advantages of voltage divider biasing of BJT.
- Explain with circuit diagram and input output waveform center trapped full wave rectifier.
- Differentiate between positive and negative feedback (any 4pts.).
- Explain RC phase shift oscillator with circuit diagram.

**6. Attempt any four of following :** **16**

- For Hartley oscillator  $C = 2 \text{ nF}$ ,  $L = 5.6 \text{ mH}$ ,  $L_z = 56 \mu \text{ H}$ . Calculate frequency of oscillation.
  - Draw circuit diagram of Colpitts Oscillator state its frequency of oscillation equation.
  - Draw and explain the basic block diagram of microprocessor.
  - Explain with circuit diagram IC 723 a dual voltage regulator.
  - Explain with circuit diagram transistor as a switch.
  - Define  $\alpha$  and  $\beta$ . Derive relation bet.  $\alpha$  and  $\beta$ .
-