

11. (a) (i) List the features of DTL logic family and explain the function of DTL NAND gate. (8)
- (ii) Explain the function of TTL logic with totem pole output configuration. (8)

Or

- (b) Explain in detail the CMOS logic circuits and CMOS transmission gates. (16)

12. (a) (i) Explain the Full subtractor. (6)
- (ii) Explain the 4 bit Adder - Subtractor using parallel load. How the detection of overflow is verified? (10)

Or

- (b) (i) Explain the function of Carry look ahead adder. (8)
- (ii) Draw and Explain the 3 bit Magnitude comparator. (8)

13. (a) (i) Explain the function of Demultiplexer and Parity checker. (8)
- (ii) Describe the Binary to Gray code converter. (8)

Or

- (b) (i) Implement the Boolean function $F(x,y,z) = \Sigma(1,2,6,7)$ using Multiplexer. (8)
- (ii) Discuss about the basics of different modeling methods. Write a Dataflow model for a 4 bit adder. (8)

14. (a) (i) Draw and Explain the block diagram of Moore and Mealy state machines. (8)
- (ii) Describe the ASM chart and explain the application of the ASM chart to design a sequential circuit with an example. (8)

Or

- (b) (i) Explain the function of a universal shift register. (8)
- (ii) Explain the function of Ring counter. (8)

15. (a) (i) Explain the primitive flow table and the reduction method. (8)
- (ii) Discuss about Races and Cycles. (8)

Or

- (b) Discuss in detail the Hazards and Hazard elimination. (16)