

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

R05 IV B.Tech. (CCC) Supplementary Examinations June – 2009

VLSI TECHNOLOGY AND DESIGN


(Electronics & Communication Engineering)

Time: 3 hours

Max Marks: 100

Answer any FIVE Questions.
All Questions carries equal marks.

 - 1.a) Briefly describe the nMOS fabrication process.
 - b) Draw a basic inverter circuit and explain its operation for nMOS.
 - c) Explain the action of BiCMOS inverter circuit. [6+6+8]
- 2.a) What is twin tub process? Explain where it used.
 - b) Compare CMOS and Bipolar technologies. [10+10]
- 3.a) Draw the stick diagram and a mask layout for an 8:1 nMOS inverter circuit. Both the input and output points should be on the polysilicon layer.
 - b) Write a brief note on inverter delays. [12+8]
- 4.a) What is sheet resistance model?
 - b) Calculate the area capacitance value with a structure occupying more than one layer as shown in the figure below. [8+12]



- 5.a) Draw a clocked inverter circuit and explain its operation.
 - b) Design a shift register with the dynamic latch operated by a two-phase clock. 8+8
- 6.a) Design a logic gate network for the full adder using multilevel logic.
 - b) Design a two bit comparator circuit using two level logic. [10+10]
- 7.a) A chip core is $3000\lambda \times 2500\lambda$ and requires 0.8A. It needs 18 signal input pads and 19 signal output pads. How many V_{DD} and V_{SS} pads are required assuming a 12λ power ring? Will the total chip size be limited by the chip core or by the pad ring?
 - b) Explain the two complementary ways to improve clock distribution. [10+10]

Contd...2

Code No: C4EC01

R05

::2::

- 8.a) Explain the fault model in CMOS designs.
- b) Write a brief note on layout design to improve testability of a circuit. [10+10]
