



III Semester B.E. (E&C) Degree Examination, Dec. 2017/Jan. 2018
(2K6 Scheme)

EE – 311 : ELECTRIC CIRCUITS AND ANALYSIS (EC)

Time : 3 Hours

Max. Marks : 100

Instruction : Answer any five questions, selecting atleast two from each Part.

PART – A

- 1. a) i) What is an ideal voltage source ?
ii) What is an ideal current source ? 4
- b) Using nodal method determine the current through the resistance of 0.5Ω connected between the nodes 1 and 2 in the network shown in the Fig. 1(b). 8

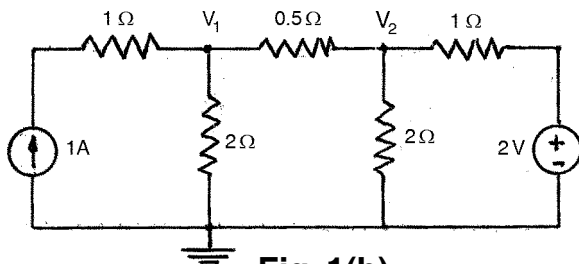


Fig. 1(b)

- c) Find E which results in zero current in $(2 + j3)\Omega$ branch of the circuit shown in Fig. 1(c) using Mesh current method. 8

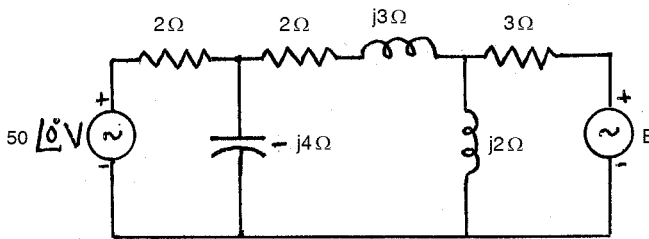


Fig. 1(c)

- 2. a) Explain dot convention in coupled circuits. 4
- b) Find equivalent inductance at terminals 1 – 1' of the network shown in Fig. 2(b). 8

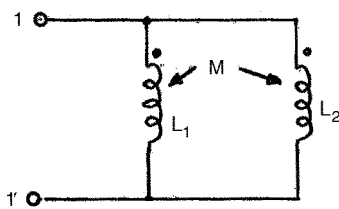


Fig. 2(b)



- c) Find the resistance between terminals A and B in the network shown in Fig. 2(c). 8

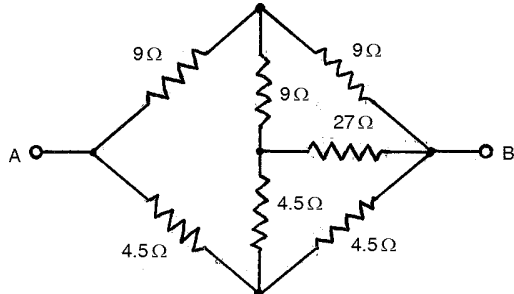


Fig. 2(c)

3. a) State and explain Thevenin's theorem. 6
 b) Find the current I in the circuit shown in Fig. 3(b) using superposition theorem. 6

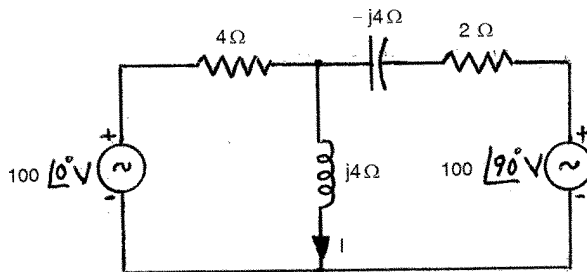


Fig. 3(b)

- c) Find Z_L for a maximum power transfer to it and hence find maximum power transferred in the circuit shown in Fig. 3(c). 8

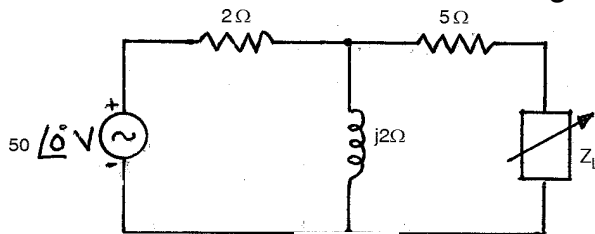


Fig. 3(c)

4. a) Show that the resonant frequency of a series RLC circuit is the geometric mean of half power frequencies. 6
 b) Determine the RLC parallel circuit parameters whose response curve is as shown in Fig. 4(b). 6

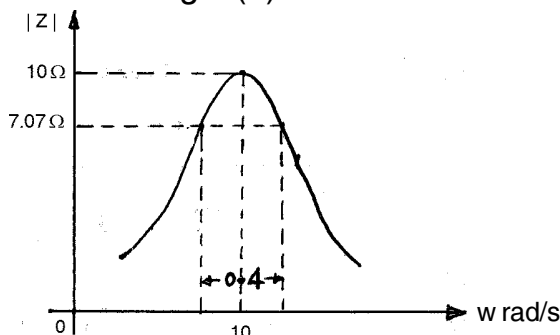


Fig. 4(b)



- c) Find the value of L for which the circuit shown in Fig. 4(c) is resonant at a frequency of 500 rad/sec.

8

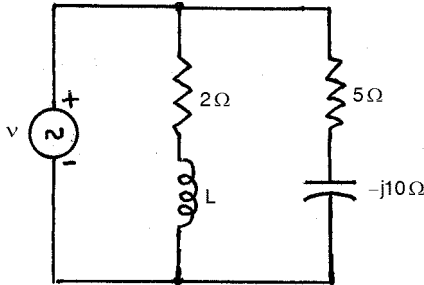


Fig. 4(c)

PART – B

5. a) State and prove :

- i) initial value theorem.
- ii) shifting theorem.

8

- b) Find the current in a series R-L-C circuit comprising of a resistor of $R = 5 \Omega$, inductance $L = 1H$ and a capacitance $C = \frac{1}{4}F$ for each of the following inputs.

- i) Ramp function $V = 12(t - 2)$
- ii) Step function $V = 3u(t - 3)$
- iii) Impulse voltage $V = 3\delta(t - 1)$.

6

- c) Find the inverse of $F(s) = \frac{s}{(s^2 + w^2)^2}$ using convolution theorem.

6

6. a) Obtain the equivalent circuits of resistance, inductance and capacitance when the equilibrium is disturbed at $t = 0$ by switching operation.

8

- b) In the network shown in the Fig. 6(b) a steady state is reached with switch K open with $V = 100$ volts, $R_1 = 10 \Omega$, $R_2 = 20 \Omega$, $R_3 = 20 \Omega$, $L = 1H$ and $C = 1 \mu F$. At time $t = 0$, the switch is closed.

- i) Write the integro-differential equations for the network after the switch is closed.
- ii) What is the voltage V_0 across C before the switch is closed ? What is its polarity ?
- iii) Solve for initial value of i_1 and i_2 at $t = 0$.

- iv) Solve for $\frac{di_1}{dt}$ and $\frac{di_2}{dt}$ at $t = 0^+$



v) Value of $\frac{di_1}{dt}$ at $t = \infty$.

12

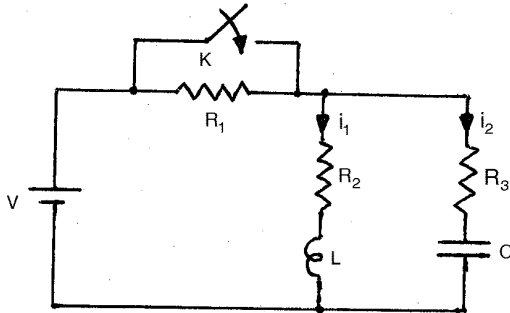


Fig. 6(b)

7. a) Define y-parameters of a 2 port network. Find the relation between Z-parameters and y-parameters.

10

b) Compute y-parameters for the network shown in the Fig. 7(b) and hence find Z-parameters.

10

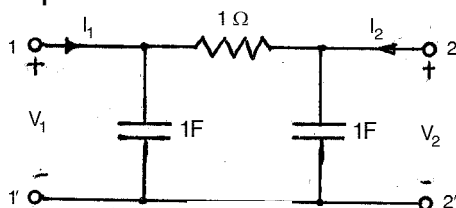


Fig. 7(b)

8. a) With a suitable network explain the following terms :

- i) Oriented graph ii) Tree iii) Cutset iv) Tieset.

4

b) In the network shown in Fig. 8(b), consider branches 1, 3 and 4 as forming a tree. Identify the link currents with the loop currents and write a tie-set schedule for the network. There from obtain equilibrium equations on loop basis.

12

$R_1 = 1 \Omega$; $R_2 = R_4 = R_6 = 2 \Omega$; $R_3 = R_5 = 3 \Omega$.

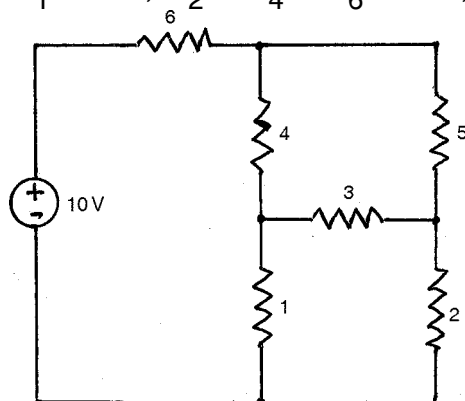


Fig. 8(b)

c) Give the duals of the following :

- i) Electric charge
- ii) Inductance
- iii) Capacitance
- iv) Flux linkage.

4