

B.E. ELECTRONICS AND TELE-COMMUNICATION ENGINEERING

2ND YEAR 1ST SEMESTER EXAM, 2019

ANALOG CIRCUITS-I

Time: Three hours


Full Marks: 100

Use a separate Answer-Script for each Part

PART-I (50 MARKS)

Answer **Q.1**, any **one** from **2 and 3** and any **one** from **4 and 5**

 1. a) Explain the function of R_G , R_{S1} and R_{S2} in Fig. 1. Determine the Q-point and show it on load line. How will the Q point be changed if R_{S2} is replaced by 220Ω . Given that $V_S = 2 \text{ V}$.
 b) Draw the small signal equivalent circuit of Fig. 1. Calculate maximum ac voltage gain, input resistance and output resistance.



2. a) Explain the function of external capacitances in IC voltage regulators. Explain short circuit protection in series voltage regulator circuit.
 b) Why negative feedback is important in wide range of OP-AMP applications.
 c) Define input offset voltage and slew rate and explain their origin.

Figure 1 [3]

d) For a step input the output of op-amp appears after $1 \mu\text{s}$. calculate its slew rate. $V_{in} =$



3. a) Design a voltage regulator using LM317 to obtain regulated voltage of 10 V. [5]
 b) Explain difference mode and common mode operation of differential amplifier using BJT. Find the expression for voltage gain, input resistance and output resistance for both cases. [5+5]

4. a) Explain the effect of noise in comparator circuits. [4]
 b) Calculate output voltage in Fig. 2. [6]
 c) Explain the temperature measurement using instrumentation amplifier [10]

 


Figure 2 [8]


5. a) Explain the function of all pass filter with circuit diagram and mention its use. [6+2]
 b) Design a all pass filter to obtain a phase shift of 90° [4]
 c) Draw and explain frequency response of practical integrator circuit. [8]

[Turn over

PART- II


Section A : Answer any TWO

 1. **Explain** the working principle of a Full Wave Voltage Multiplier with proper circuit diagram. **Plot** the initial voltage across both the capacitors and the overall output voltage for a sinusoidal input (*assume ideal diode and capacitors are uncharged initially*).
[Marks: 4+6=10]
2. A full wave transformer coupled rectifier with $R_L = 20k\Omega$ is implemented using ideal diodes. Find the value of V_{dc} , V_{rms} and V_{rrms} (ripple rms). **Design** one capacitive filter (*find the value of the capacitor*) to reduce the peak to peak ripple voltage across load within 1% of DC output.
[Marks: 6+4=10]
3. Find the output voltage V_o of the diode circuit shown in Figure 1 and **plot** the output voltage for a temperature range 0 to 100°C. [*All diodes are real and identical*]
[Marks: 6+4=10]



Section B : Compulsory

 4. **Determine** the expression of stability factor $S(I_{co})$ for a BJT in Emitter Bias configuration. **Calculate** the value of $S(I_{co})$ of the voltage divider circuit shown in Figure 2. [$\beta = 100$, $R_1 = 60k\Omega$, $R_2 = 30k\Omega$, $R_E = 3k\Omega$, $R_C = 1k\Omega$, and $V_{CC} = 12V$]
[Marks: 5+5=10]



Section C : Answer any TWO

5. **Explain** the working principle of a current mirror circuit. **Design** one current mirror with $1\mu\text{A}$ current in primary branch and $2\mu\text{A}$ and $2.5\mu\text{A}$ in two different secondary branches. (Available transistors are identical with $\beta=1000$ and $V_{BE}=0.7\text{V}$. Supply voltage 3V) [Marks: 4+6=10]
6. A CE amplifier with proper biasing arrangement is shown in Figure 3. [$\beta=100$, $C_E=C_C=C_B=1\mu\text{F}$ and neglect r_o]
 A) **Draw** the small signal model of the entire amplifier and **calculate** the midband gain.
 B) **Find** all the low frequency poles, zeros and lower cut-off frequency due to coupling capacitors.
 C) **Plot** the gain response with respect to frequency for very low to mid frequency range. [Marks: 5+3+2=10]
7. Using the high frequency model of BJT find the expression of $\beta(s)$, ω_β and ω_T .
Calculate the value of ω_β and ω_T for the BJT shown in figure 3. [use $\beta=100$, $C_\pi=12\text{pF}$, $C_C=2\text{pF}$] [Marks: 6+4=10]

