 


**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER– III (New) EXAMINATION – WINTER 2019****Subject Code: 3131704****Date: 26/11/2019****Subject Name: Digital Electronics****Time: 02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		<b>MARKS</b>
<b>Q.1</b>	(a) Give the comparison of 1's and 2's complements.	<b>03</b>
	(b) Explain De Morgan's theorem with suitable example.	<b>04</b>
	(c) Explain the commutative law, associative law, and distributive law in Boolean algebra with example	<b>07</b>
<b>Q.2</b>	(a) Convert $(163.875)_{10}$ to binary.	<b>03</b>
	(b) Design Full Adder using two Half Adder and one two input OR gate.	<b>04</b>
	(c) Implement the following function with 8:1 multiplexer: $F(A, B, C, D) = \sum(0, 1, 3, 4, 8, 9, 15)$	<b>07</b>
<b>OR</b>		
	(c) Explain the working of 4:1 multiplexer.	<b>07</b>
<b>Q.3</b>	(a) What do you mean by universal gates? Implement NOT, AND, OR with any one universal gate.	<b>03</b>
	(b) Implement 4 bit Shift Register for 1010 binary pattern.	<b>04</b>
	(c) A combinational circuit is defined by functions: $F_1(A, B, C) = \sum m(3, 5, 6, 7)$ $F_2(A, B, C) = \sum m(0, 2, 4, 7)$ Implement the circuit with PLA having three inputs, four product terms and two outputs.	<b>07</b>
<b>OR</b>		
<b>Q.3</b>	(a) Explain the operation of master slave J-K flip flop.	<b>03</b>
	(b) Explain gray code in detail.	<b>04</b>
	(c) Design a type T counter for given state diagram	<b>07</b>



<b>Q.4</b>	(a) Describe Fan In, Noise Margin and Propagation Delay parameters for digital IC.	<b>03</b>
	(b) Explain ROM with block diagram. Give classification of ROM.	<b>04</b>
	(c) Design 3 to 8 line decoder with neat sketch and truth table.	<b>07</b>
<b>OR</b>		
<b>Q.4</b>	(a) Simplify Boolean function $F = A'B'C' + B'CD' + A'BCD' + AB'C'$ using K map.	<b>03</b>
	(b) Explain TTL gate with Totem pole output.	<b>04</b>

- (c) Explain 4 bit magnitude comparator with necessary Boolean expression. **07**
- Q.5** (a) Explain D flip-flop. **03**  
 (b) Explain arithmetic ,logic micro operation. **04**  
 (c) Minimize the following function using tabulation method: **07**  
 $F(w, x, y, z) = \sum (1, 4, 6, 7, 8, 9, 10, 11, 15)$
- OR**
- Q.5** (a) Design full subtracter with necessary derivation of functions. **03**  
 (b) Explain the following register transfer operation with the help of necessary diagram **04**  
 T1: C ← A  
 T2: C ← B  
 Assume A, B and C are 4 – bit registers.
- (c) Simplify the Boolean expression  $F(A,B,C,D) = \sum(2,3,6,7,8,10,11,13,14)$  using K Map. **07**

\*\*\*\*\*