

17215

11920

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--


- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Illustrate your answers with neat sketches wherever necessary.
  - (3) Figures to the right indicate full marks.
  - (4) Assume suitable data, if necessary.
  - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

1. Attempt any TEN :

20

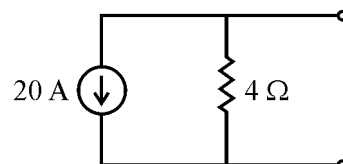- (a) Draw B-H curve for hard and soft magnetic material.
- (b) Define self inductance and mutual inductance.
- (c) Draw the constructional diagram of PVC gang capacitor.
- (d) Define PIV and TUF w.r.t. rectifiers.
- (e) State different types of filters used in rectifiers.
- (f) State superposition theorem.
- (g) Draw Ideal and Practical current source.
- (h) Convert following current source to its equivalent voltage source :




[1 of 4]

P.T.O.

- (i) Draw the symbol of Tunnel diode and Schottky diode.
  - (j) Write four applications of Zener diode.
  - (k) Draw the circuit diagram of RC integrator. Draw nature of output signal for sine wave input.
  - (l) Write two applications of clippers and two applications of clampers.
- 2. Attempt any FOUR :** **16**
- (a) Explain the working of TDR along with its symbol and characteristics.
  - (b) Compare linear and logarithmic potentiometer.
  - (c) Draw the constructional diagram of electrolytic capacitor and explain the working.
  - (d) Describe working of variable air gang capacitor.
  - (e) Describe working of slug tuned inductor with neat sketch.
  - (f) Explain operation of tunnel diode with its characteristics.
- 3. Attempt any FOUR :** **16**
- (a) Compare Avalanche breakdown and Zener breakdown.
  - (b) Describe the working of PN junction diode with the help of its VI characteristics.
  - (c) Describe the operating principle of LASER diode with neat sketch.
  - (d) Enlist four specification of Zener diode.
  - (e) State the values of following with respect to HWR :
    - (i) Ripple factor
    - (ii) Ripple frequency
    - (iii) TUF
    - (iv) Efficiency
  - (f) Compare half wave rectifier and center tapped full wave rectifier with respect to
    - (i) No. of diodes
    - (ii) PIV
    - (iii) Nature of output waveform
    - (iv) Efficiency
- 4. Attempt any FOUR :** **16**
- (a) Describe the working of full wave rectifier with input and output waveforms.
  - (b) Calculate values of capacitor if following is printed on body of capacitor :
    - (i) 104
    - (ii) 3k3

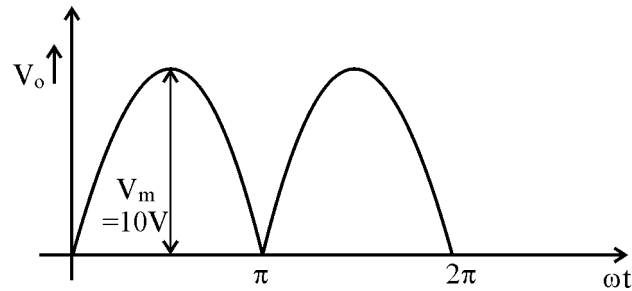- (c) Draw circuit diagram of capacitor filter with bridge rectifier. Explain it with input-output waveforms.
- (d) In FWR  $V_M = 10V$ ,  $R_L = 10\text{ k}\Omega$ , calculate  $V_{DC}$ ,  $I_{DC}$  and ripple factor.




- (e) State operating principle of LED. Write material names used to manufacture LED.
- (f) Compare PN-Junction and Zener diode.

**5. Attempt any FOUR :**

**16**

- (a) Explain operation of combinational clipper with neat circuit diagram and waveforms.
- (b) Describe the working principle of RC differentiator with neat sketch.
- (c) State and explain Norton's theorem with example.
- (d) Identify the following circuit shown in Figure. Draw input and output waveforms.

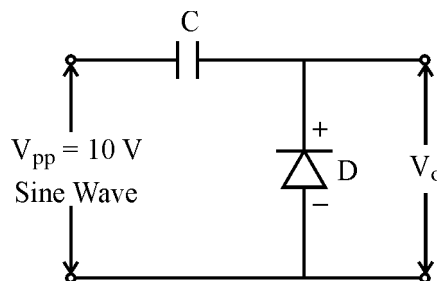


**Figure No. 3**

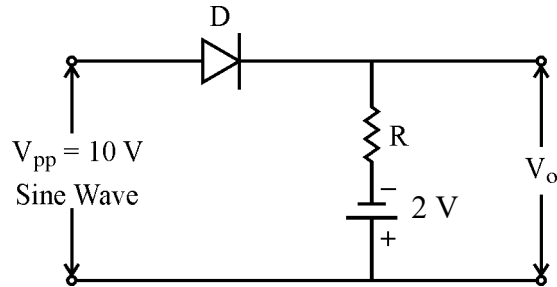
- (e) State the following :
- Kirchoff's voltage law
  - Kirchoff's current law
- (f) Define the following terms :
- Active Network
  - Linear Network
  - Bilateral Network
  - Unilateral Network

6. Attempt any FOUR :


- (a) Compare clipper and clamper.
- (b) Identify the circuit shown in Figure. Draw input and output waveforms.



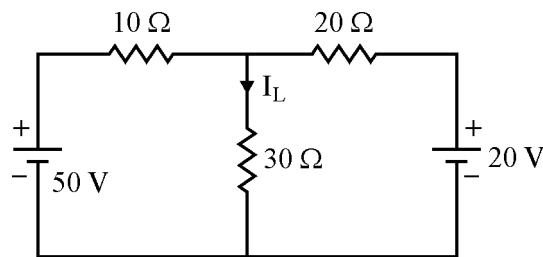
- (c) Calculate  $I_L$  for the network shown in Figure.



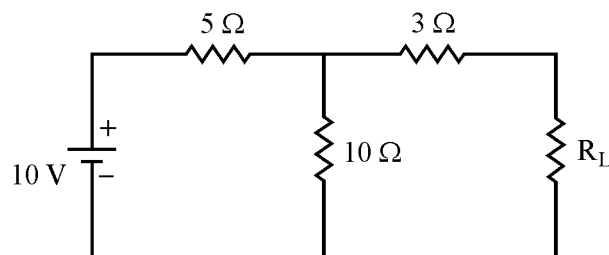- (d) Find the value of load resistance  $R_L$  to get maximum power transferred to it.



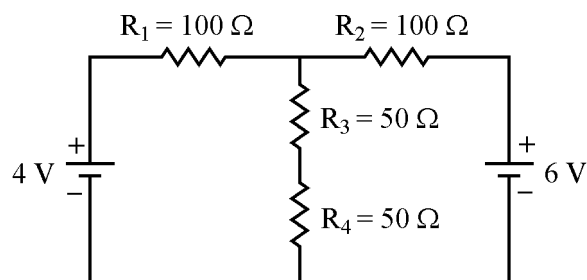- (e) Find current through  $R_4$  using superposition theorem.



- (f) State the meaning of term open circuit and short circuit with neat diagram.

---